

Simple Electronic Circuit Breaker

This circuit uses the on-resistance of the MOSFET as the current sensor. Reset it by removing the input power or the load. The circuit draws no current unless tripped.

Andrew R. Morris
morr3763@bellsouth.net

